# sEKV Parameter Extraction for the Generic 180nm Process

**Long-channel nMOS (Version 1)**

02.10.2026

In this notebook we extract the sEKV parameters for a long-channel nMOS transistor from the data generated with the EKV 2.6 compact model for a generic 180nm CMOS process.

# Table of contents

**1 Introduction** **4**

**2 Transistor geometry parameters** **5**
2.1 Effective length and width for current . . . . . 5

**3 DC Transfer Characteristic Parameters** **6**
3.1 Generating and importing the data . . . . . 6
3.1.1 $I_D$ and $G_m$ versus $V_G$ . . . . . 6
3.1.2 $G_m$-$V_G$ and $G_m$-$I_D$ . . . . . 7
3.2 Filtering the outliers . . . . . 7
3.3 Direct extraction with $\lambda_c = 0$ . . . . . 10
3.3.1 Slope factor $n$ and $I_{spec}$ extraction . . . . . 10
3.3.2 Threshold voltage extraction . . . . . 12
3.3.3 Summary . . . . . 15
3.4 Extraction using curve fitting with $\lambda_c = 0$ . . . . . 17
3.4.1 Slope factor $n$ and $I_{spec}$ extraction . . . . . 17
3.5 Comparison with parameters extracted from the EKV 2.6 compact model . . . . . 17

**4 Output characteristic** **20**
4.1 Generating and importing the data . . . . . 20
4.1.1 $I_D$ and $G_{ds}$ versus $V_D$ . . . . . 20
4.1.2 Filtering the outliers . . . . . 21
4.2 Extracting the CLM parameter . . . . . 21

**5 Noise** **23**
5.1 Setting the bias conditions . . . . . 23
5.2 Extract operating point information . . . . . 23
5.3 Input-referred noise PSD . . . . . 24

**6 Conclusion** **26**

**References** **27**

*© C. Enz under CC BY-NC-SA* 

# 1 Introduction

In this notebook we will extract the sEKV parameters [1] [2] for a long-channel nMOS transistors from a generic 180nm bulk CMOS process. The physical parameters are given in Table 1.1, the global process parameters in Table 1.2.

Table 1.1: Physical parameters

| Parameter | Value | Unit |
|---|---|---|
| $T$ | 300 | $K$ |
| $U_T$ | 25.875 | $mV$ |

Table 1.2: Global process parameters

| Parameter | Value | Unit |
|---|---|---|
| $V_{DD}$ | 1.8 | $V$ |
| $C_{ox}$ | 8.46 | $\frac{fF}{\mu m^2}$ |
| $W_{min}$ | 200 | $nm$ |
| $L_{min}$ | 180 | $nm$ |

The easiest way to extract the sEKV parameters is to use the python tool developed by H.C. Han and available on GitLab [3]. The tool and the extraction procedure are described in [4]. In this notebook we will detail the extraction procedure and show how the parameters can be extracted manually.

We start by looking at the channel width and length corrections for the drain current and for the capacitances. Then we will extract the sEKV parameter using a direct extraction methodology with the velocity parameter $\lambda_c = 0$. We then will extract the additional parameter $\lambda_c$ using a direct extraction methodology. Then we will extract all the sEKV parameters by optimization using nonlinear curve fitting.

We also will extract the output conductance due to channel-length modulation (CLM) and the related parameter.

Finally, we will check the white noise model and extract the EKV flicker noise parameters.

The extracted parameters are then all saved in an Excel worksheet.

© C. Enz under CC BY-NC-SA 

# 2 Transistor geometry parameters

## 2.1 Effective length and width for current

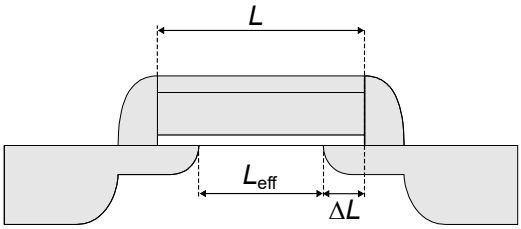



Figure 2.1: Definition of the effective length.

The effective length and width in the EKV 2.6 compact model are defined as [5]

$$W_{eff} = W + \Delta W, \tag{2.1}$$
$$L_{eff} = L + \Delta L, \tag{2.2}$$

where the width and length correction parameters $\Delta W$ and $\Delta L$ are given in Table 2.1.

Table 2.1: Transistor geometry.

| Parameter | Symbol | Value | Unit |
|---|---|---|---|
| Selected transistor width and length | | | |
| Width | $W$ | 10 | $\mu m$ |
| Length | $L$ | 10 | $\mu m$ |
| Width and length correction parameters | | | |
| Width correction | $\Delta W$ | 39 | $nm$ |
| Length correction | $\Delta L$ | -76 | $nm$ |
| Selected transistor effective width and length | | | |
| Effective width | $W_{eff}$ | 10.039 | $\mu m$ |
| Effective length | $L_{eff}$ | 9.924 | $\mu m$ |

© C. Enz under CC BY-NC-SA 

# 3 DC Transfer Characteristic Parameters

## 3.1 Generating and importing the data

The data used for the sEKV parameters extraction is generated by simulation with ngspice using the EKV 2.6 compact model [5] for a generic 180nm bulk CMOS process. We present the $I_D$-$V_G$ and $G_m$-$V_G$ data below.

### 3.1.1 $I_D$ and $G_m$ versus $V_G$

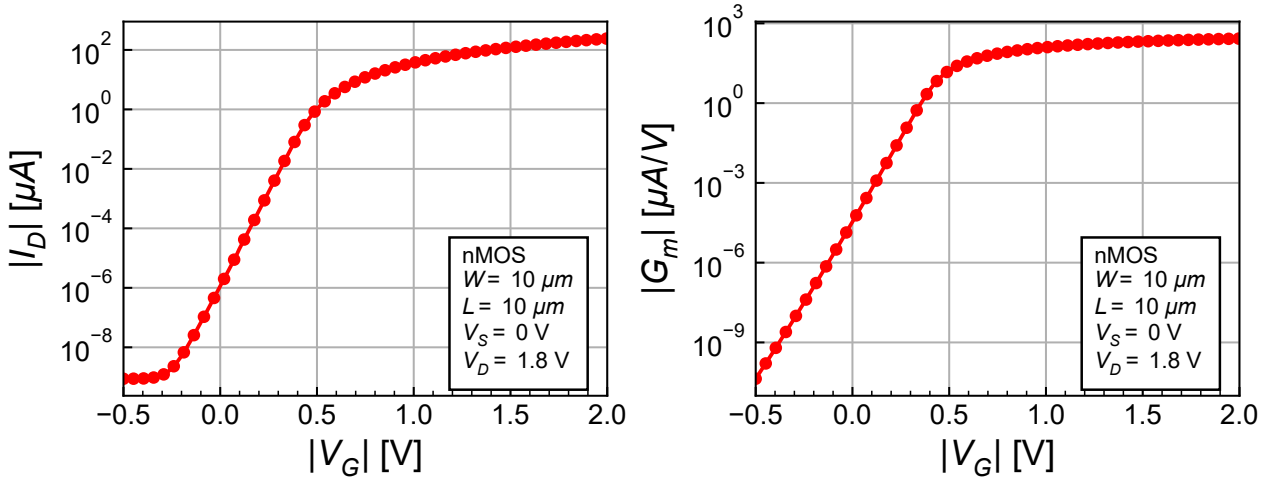



Figure 3.1: Imported $I_D$-$V_G$ and $G_m$-$V_G$.

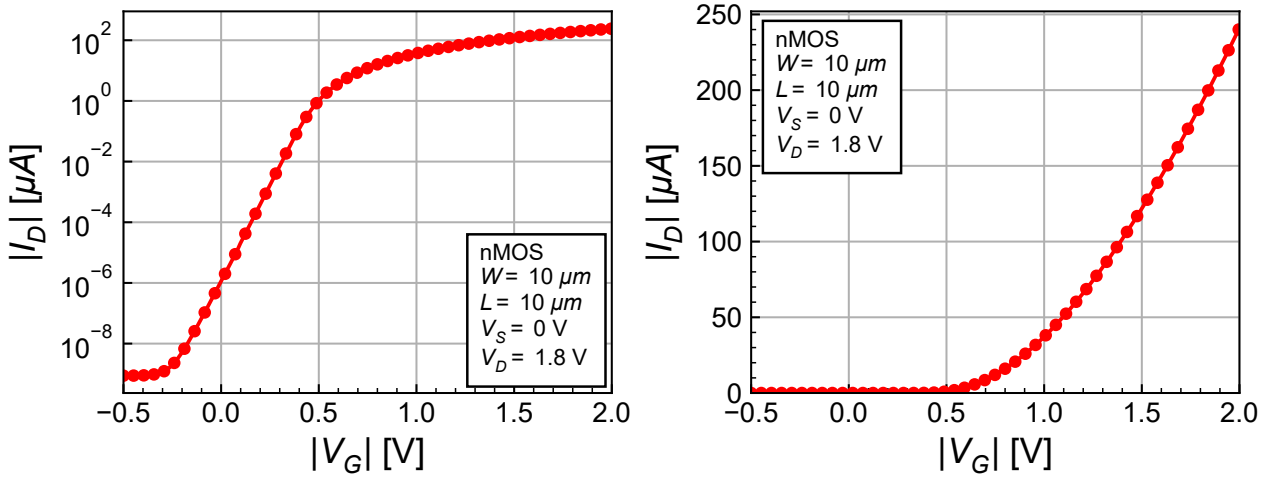



Figure 3.2: Imported $I_D$-$V_G$.

© C. Enz under CC BY-NC-SA 

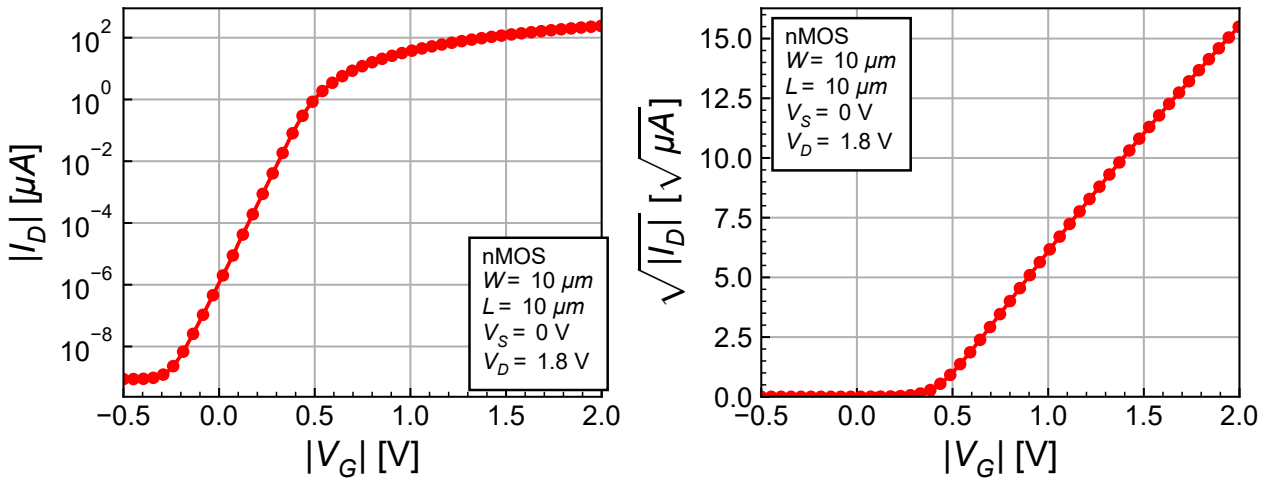



Figure 3.3: Imported $I_D$-$V_G$.

### 3.1.2 $G_m$-$V_G$ and $G_m$-$I_D$

We now will check the derivative namely the gate transconductance obtained from the simulator and compare it to the numerical differentiation of the large-signal $I_D$-$V_G$ characteristic.

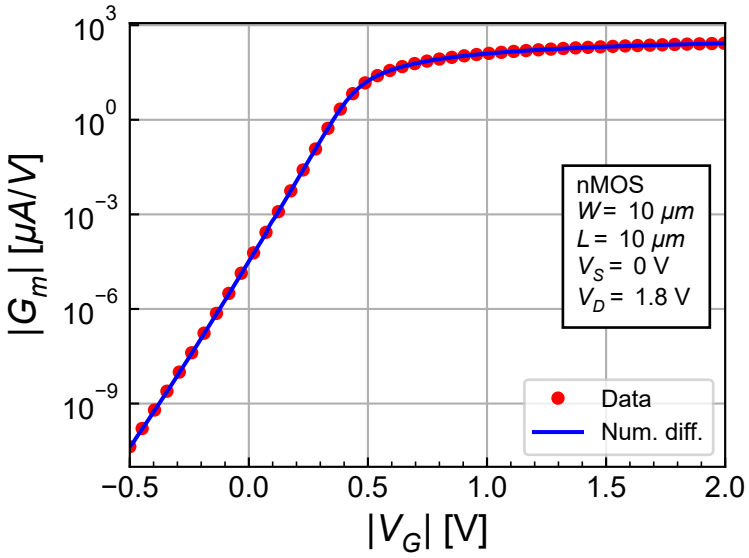



Figure 3.4: Check of the $G_m$-$V_G$ consistency.

We see that the transconductance obtained by differentiating the large-signal $I_D$-$V_G$ characteristic is equal to the transconductance extracted from the EKV 2.6 compact model. We will keep the value extracted from the EKV 2.6 compact model.

## 3.2 Filtering the outliers

Since the sEKV model [2] doesn't account for leakage currents such as gate induced drain leakage (GIDL) that appears at very low current, we need to filter the outlier points. This is done below with the outlier points shown in blue and the points used for the extraction shown in red.

We can now proceed with the parameter extraction, starting with the direct extraction approach.

© C. Enz under CC BY-NC-SA 

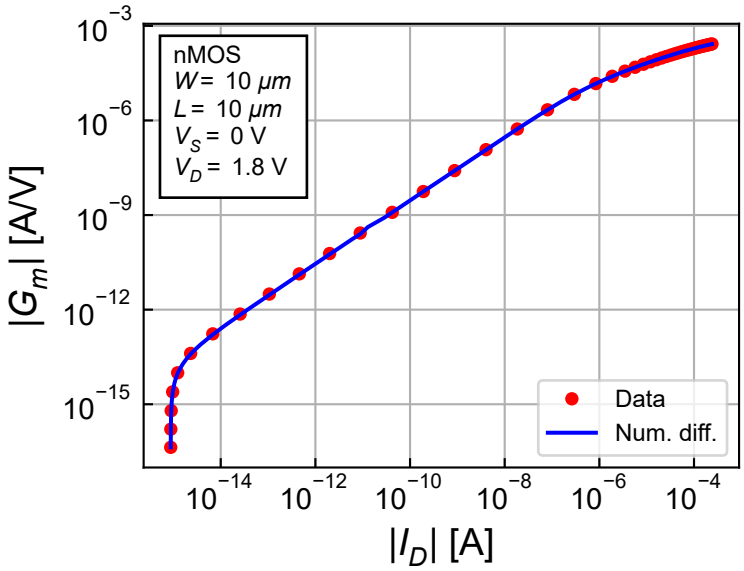



Figure 3.5: Check of the $G_m$-$I_D$ consistency.

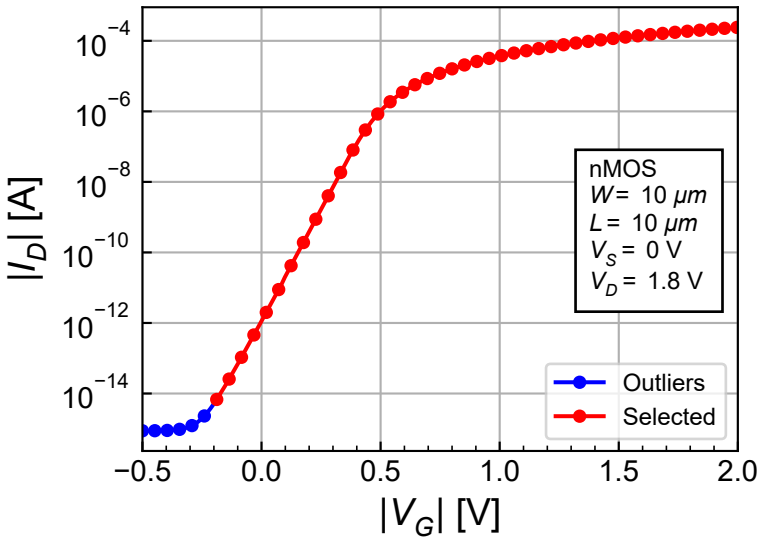



Figure 3.6: Filtering the outliers from the $I_D$-$V_G$ charactersitic.

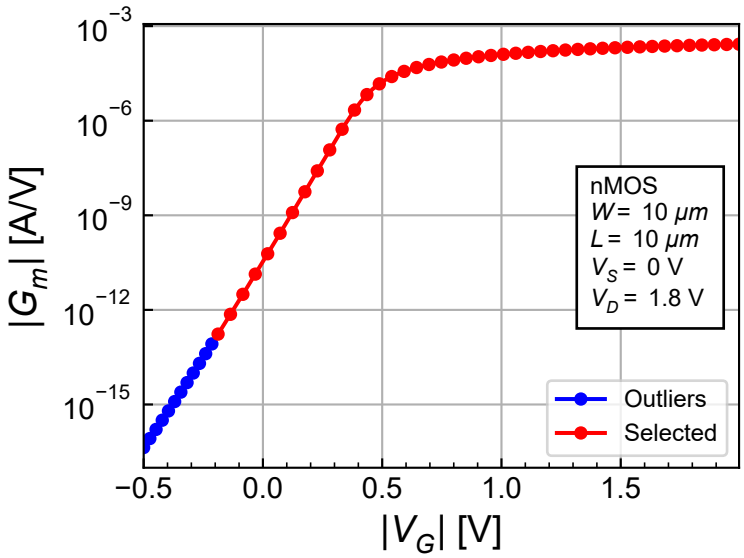



Figure 3.7: Filtering the outliers from the $G_m$-$V_G$ charactersitic.

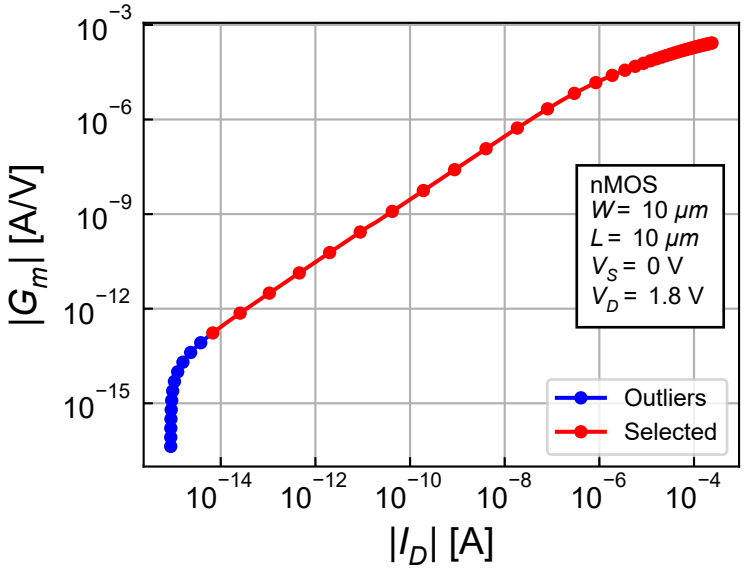



Figure 3.8: Filtering the outliers from the $G_m$-$I_D$ charactersitic.

## 3.3 Direct extraction with $\lambda_c = 0$

In the direct extraction approach, we avoid using curve fitting or optimization and manipulate the data to extract a given parameter in a certain data range.

### 3.3.1 Slope factor $n$ and $I_{spec}$ extraction

The gate transconductance in weak inversion and saturation is given by [1]

$$G_m = \frac{I_D}{n\,U_T}. \tag{3.1}$$

So if we plot $I_D/(G_m\,U_T)$ we should see a plateau in weak inversion the value of which is equal to the slope factor $n$.

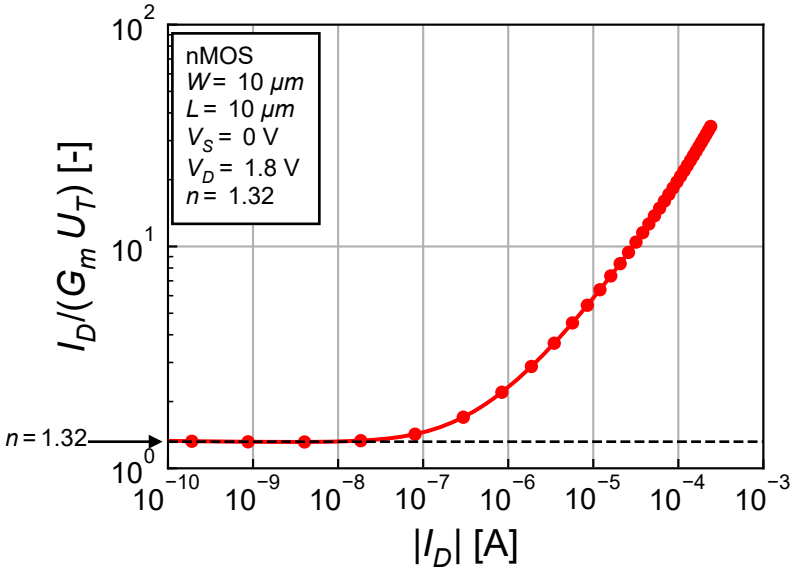



Figure 3.9: Slope factor extraction.

This is illustrated in Figure 3.9 resulting in $n = 1.32$. On the other hand the normalized $G_m/I_D$ function for a long-channel transistor in strong inversion and saturation is given by [1]

$$\frac{G_m\,n\,U_T}{I_D} = \frac{1}{\sqrt{IC}} = \sqrt{\frac{I_{spec}}{I_D}}. \tag{3.2}$$

We can then plot $(G_m\,n\,U_T)^2/I_D$ which should find a maximum value equal to $I_{spec}$.

This is illustrated in Figure 3.10 resulting in $I_{spec} = 514\ nA$ corresponding to $I_{spec\square} = 508\ nA$. We can now plot $I_D/(G_m\,U_T)$ versus $I_D$ as shown in Figure 3.11. We clearly see the two asymptotes in weak (i.e. $I_D < I_{spec}$) and strong inversion (i.e. $I_D > I_{spec}$).

Having extracted $n$ and $I_{spec}$, we can now plot the normalized $G_m/I_D$ function versus $IC$ which is shown in Figure 3.12.

The fit is reasonable over the entire $IC$ span. There is some discrepancy in the strong inversion region which is due to the mobility reduction due to the vertical field appearing for $IC > 10^2$. The latter can be accounted for by using the $\lambda_c$ parameter which is normally used for modeling the effect of velocity saturation in short-channel transistor but can also be used to correct the effect of mobility reduction due to the vertical field appearing in long-channel transistors. We will not do this here since we want to extract the long-channel parameters keeping $\lambda_c = 0$, but since we are mostly interested in

© C. Enz under CC BY-NC-SA 

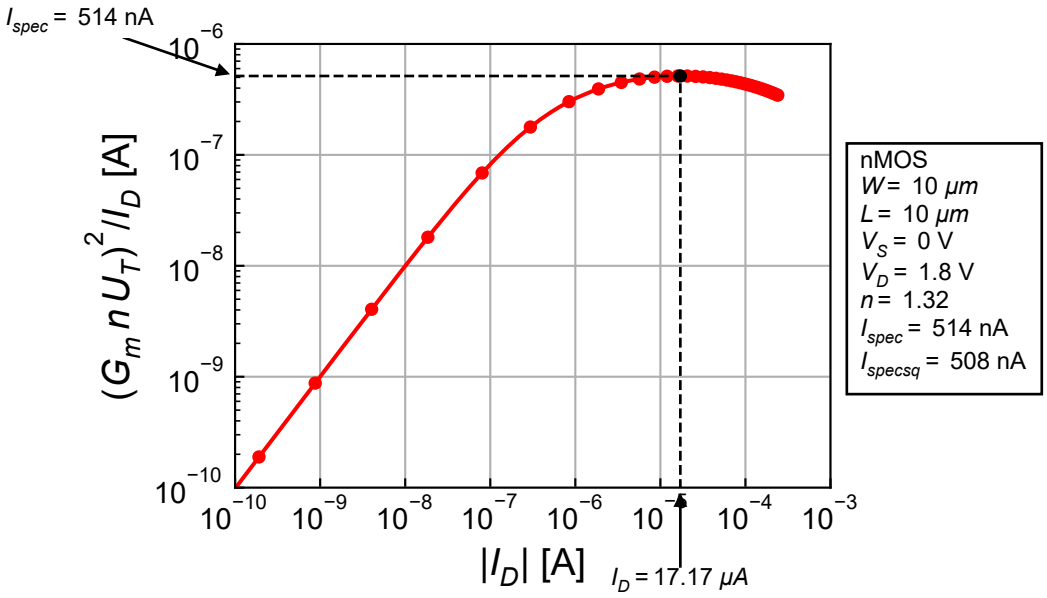



Figure 3.10: $I_{spec}$ extraction.

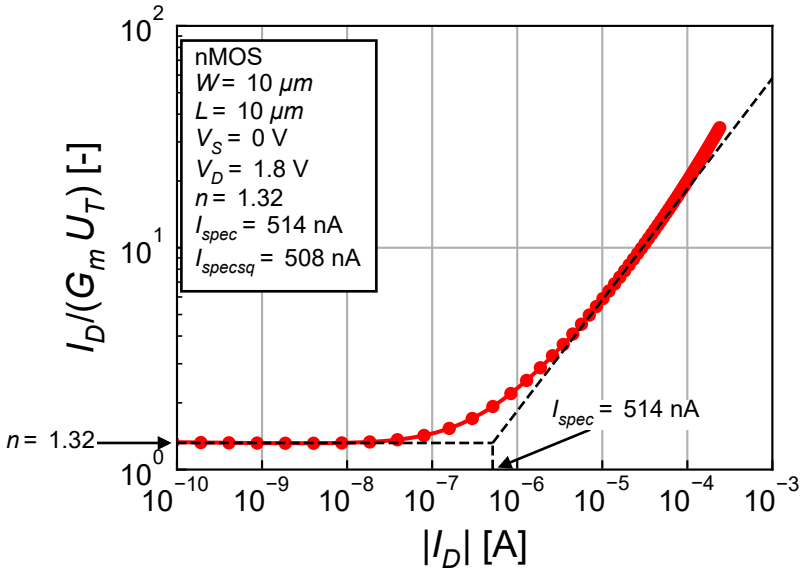



Figure 3.11: $n$ and $I_{spec}$ check.

© C. Enz under CC BY-NC-SA 

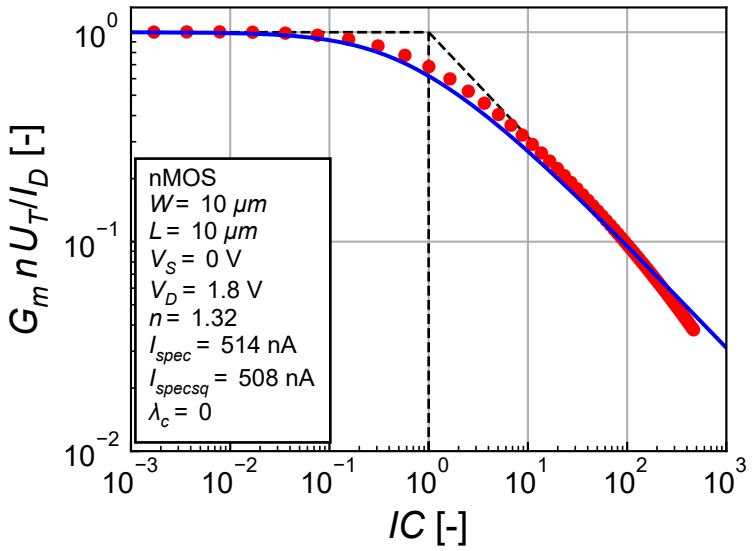



Figure 3.12: Resulting normalized $G_m/I_D$ characteristic.

the moderate inversion region, we can slightly increase $I_{spec}$ to improve the fit in moderate inversion at the cost of a degradation in strong inversion. This results in the normalized $G_m/I_D$ function versus $IC$ shown in Figure 3.13.

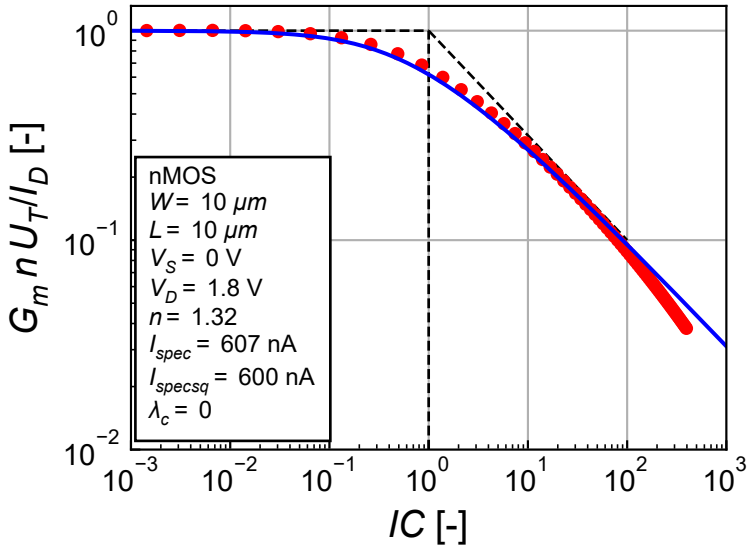



Figure 3.13: Fine tuning of the normalized $G_m/I_D$ function versus $IC$ in moderate inversion.

The fit is now much better in moderate inversion but less in strong inversion. This is due to mobility reduction due to the vertical field which is an effect that is not accounted for in the model. However, it offers a good trade-off between moderate inversion (where the curve is slightly below the simulations) and strong inversion up to $IC = 100$ (where the simulation points are slightly below the curve). We therefore will keep the new value of $I_{spec\square}$, namely $I_{spec\square} = 600\ nA$.

### 3.3.2 Threshold voltage extraction

We can extract the threshold voltage in weak inversion (assuming $V_S = 0$) from the normalized current (inversion coefficient) given by [1]

$$IC = e^{\frac{V_G - V_{T0}}{nU_T}}. \tag{3.3}$$

We can now plot

$$V_{T0} = V_G - nU_T \ln(IC) \tag{3.4}$$

to extract the threshold voltage. This results in the plot shown in Figure 3.14.

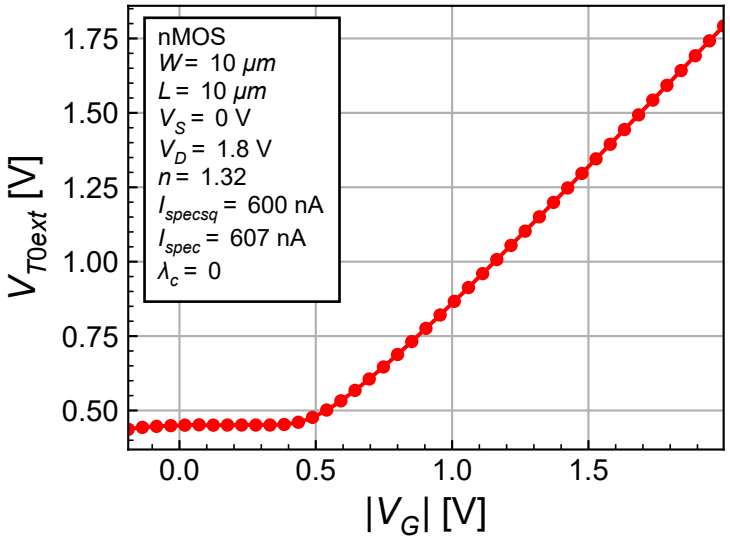



Figure 3.14: Threshold voltage extraction.

We see a plateau in weak inversion where we can average its value to get the threshold voltage in weak inversion which we can zoom into as shown in Figure 3.15.

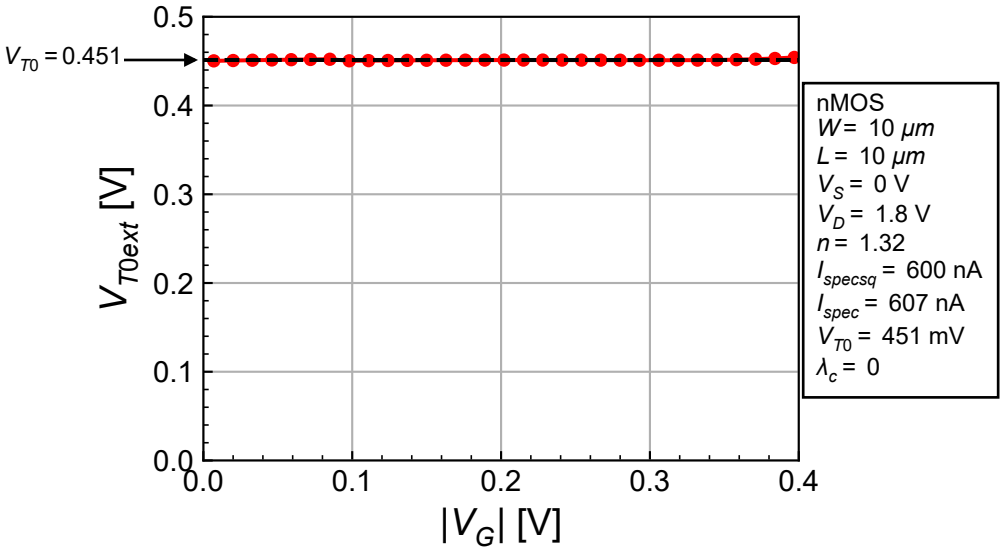



Figure 3.15: Threshold voltage extraction in weak inversion.

The average value of $V_{T0} =$ in this range is given by $V_{T0} = 451\ mV$.

We can now plot the $I_D$-$V_G$ for the extracted parameters which is shown in Figure 3.16.

The fit is good, but $I_{spec}$ can be slightly reduced.

We get a reasonable fit with some deviations in strong inversion, which is expected since we focused on the moderate inversion and kept $\lambda_c = 0$. Anyway, when designing circuits we rarely we use an inversion coefficient larger than 100 corresponding for this technology to an overdrive voltage $V_G - V_{T0} \cong 0.7\,V$. The fit within this range is therefore acceptable.

© C. Enz under CC BY-NC-SA 

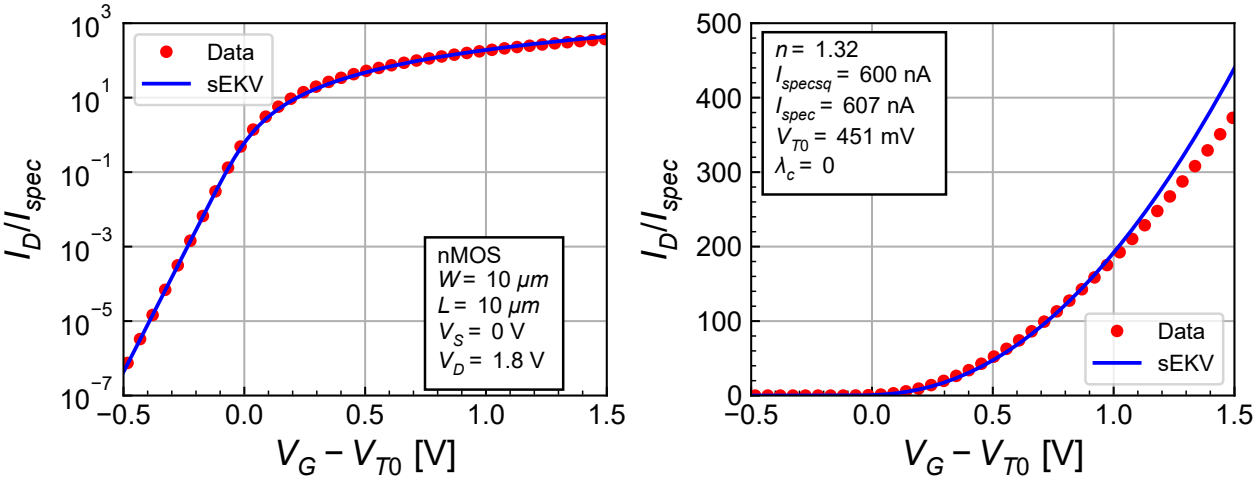



Figure 3.16: $I_D$-$V_G$ for the extracted parameters.

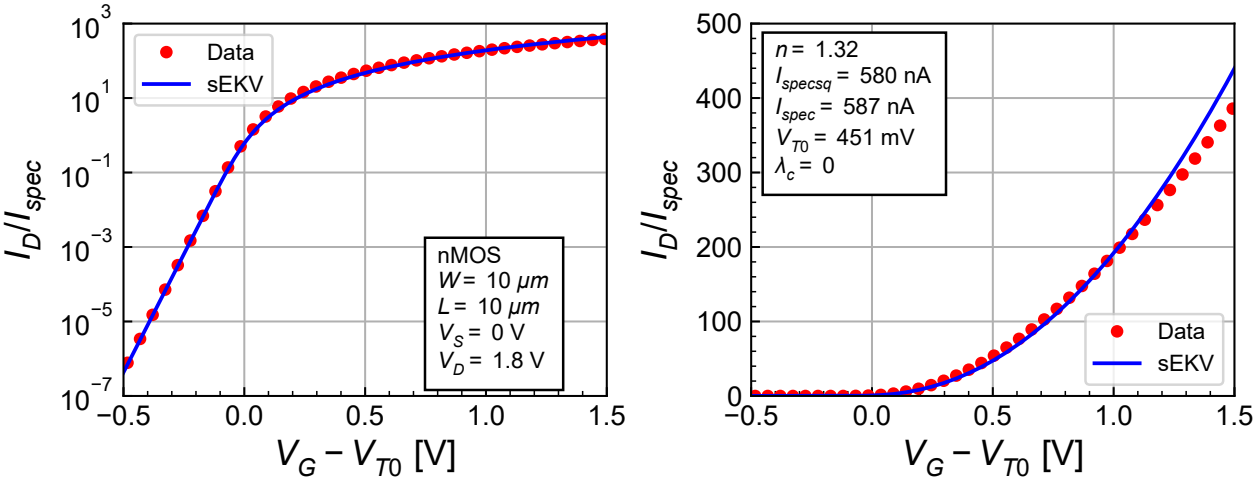



Figure 3.17: $I_D$-$V_G$ for the extracted parameters.

© C. Enz under CC BY-NC-SA 

We can also extract the threshold voltage in strong inversion by plotting $\sqrt{I_D}$ versus $V_G$ as shown in Figure 3.18.

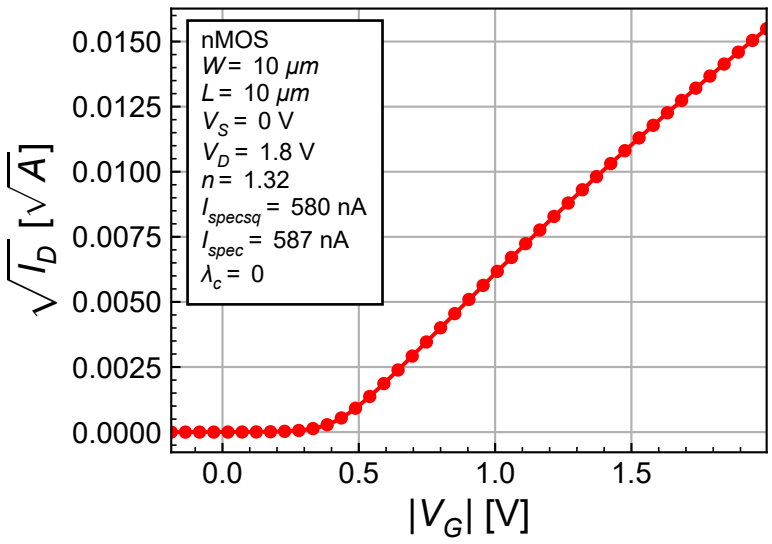



Figure 3.18: $\sqrt{I_D}$-$V_G$ for the extracted parameters.

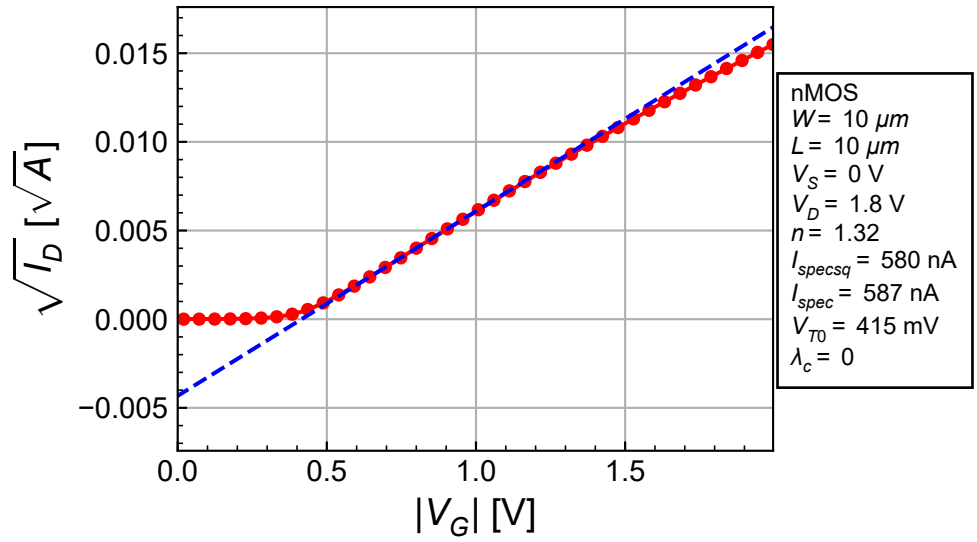



Figure 3.19: Threshold voltage extraction from $\sqrt{I_D}$-$V_G$ in strong inversion.

We can then fit the linear portion and extract the intersection point on the $V_G$ axis as shown in Figure 3.19 which results in $V_{T0} = 415\ mV$. We get a very small threshold voltage even smaller than the value extracted in weak inversion. We can check the $I_D$-$V_G$ charactersitic with this extracted threshold voltage in Figure 3.20.

As expected, we get a less good fit in weak inversion. We therefore keep the value of the threshold voltage extracted in weak inversion, namely $V_{T0} = 451\ mV$.

### 3.3.3 Summary

The results of the direct extraction method is shown in Figure 3.21, which includes the large-signal $IC = I_D/I_{spec}$ versus $V_G - V_{T0}$ on the left and the small-signal parameters $G_{ms}/G_{spec}$ versus $IC$ and $G_m\, n\, U_T/I_D$ versus $IC$ on the right. We see a good fit of the large- and small-signal parameters except in very strong inversion (i.e. $100 < IC$). The extracted parameters are summarized in Table 3.1.

© C. Enz under CC BY-NC-SA 

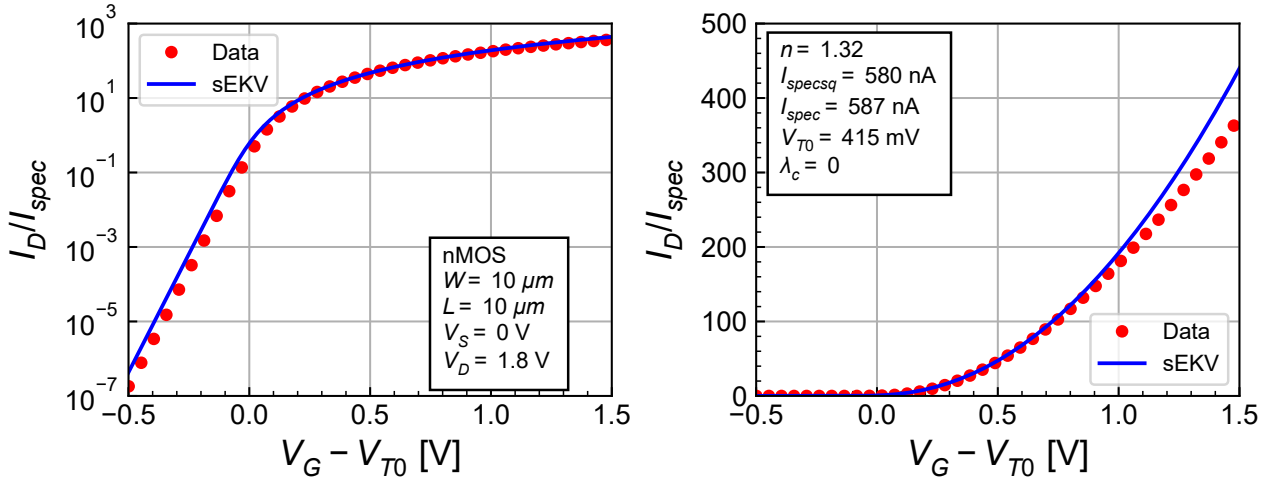



Figure 3.20: $I_D$-$V_G$ for the extracted threshold voltage.

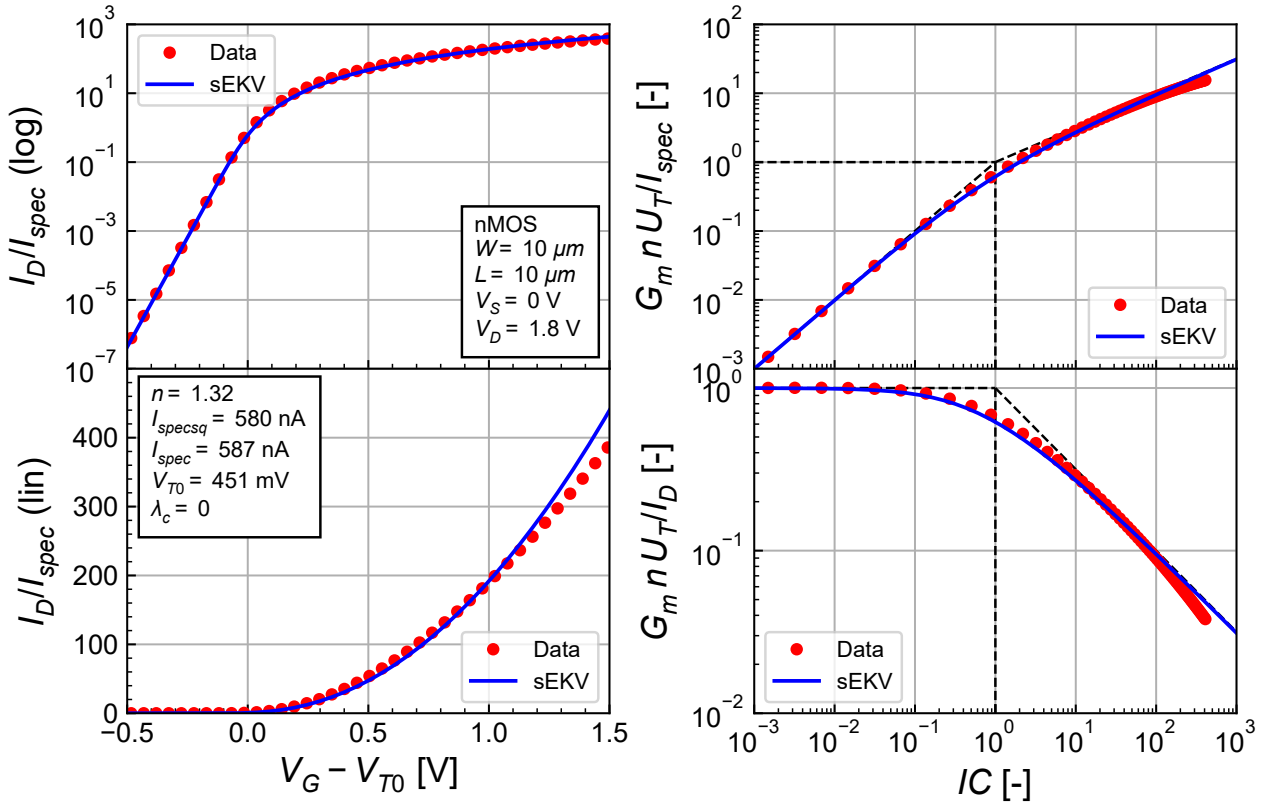



Figure 3.21: Summary of direct extraction with $\lambda_c = 0$.

© C. Enz under CC BY-NC-SA 

Table 3.1: Direct extraction of the sEKV parameters with $\lambda_c = 0$.

| Type | $n$ | $I_{spec\square}$ $[nA]$ | $V_{T0}$ $[mV]$ | $\lambda_c$ | $L_{sat}$ $[nm]$ | Comment |
|---|---|---|---|---|---|---|
| nMOS | 1.32 | 580 | 451 | 0 | 0 | direct with $\lambda_c = 0$ |

## 3.4 Extraction using curve fitting with $\lambda_c = 0$

### 3.4.1 Slope factor $n$ and $I_{spec}$ extraction

We can extract $I_{spec}$ and $V_{T0}$ for a long-channel directly from $\ln(I_D)$-$V_G$ data using curve fitting keeping $\lambda_c = 0$ and using the vlaue of the slope factor extracted above. The result is shown in Figure 3.22.

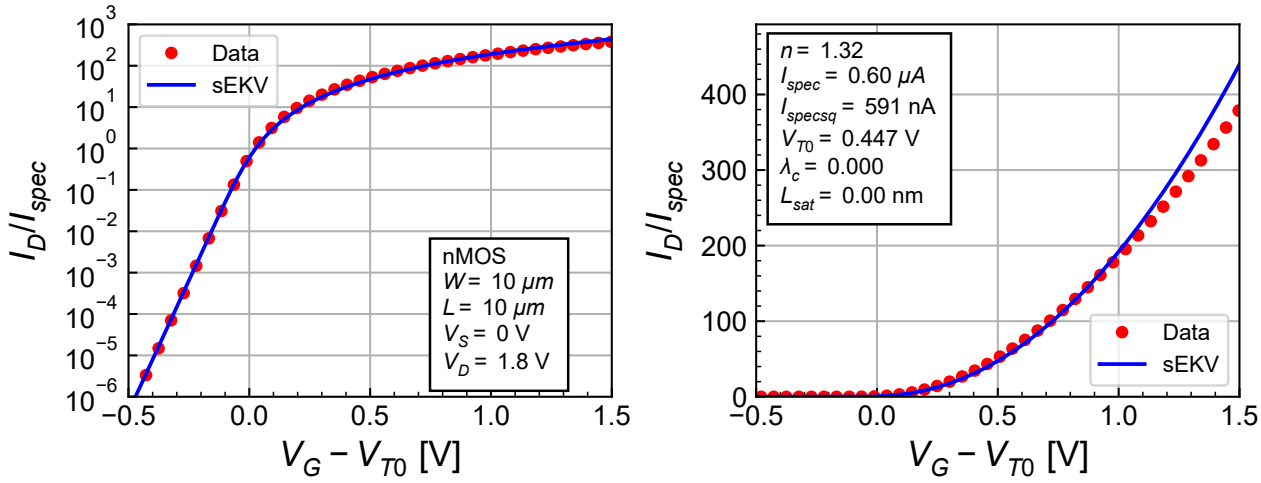



Figure 3.22: Extraction of $I_{spec}$ and $V_{T0}$ by curve fitting.

The fit is very good, remembering that $\lambda_c = 0$.

Table 3.2: Extraction of the sEKV parameters using curve fitting with $\lambda_c = 0$.

| Type | $n$ | $I_{spec\square}$ $[nA]$ | $V_{T0}$ $[mV]$ | $\lambda_c$ | $L_{sat}$ $[nm]$ | Comment |
|---|---|---|---|---|---|---|
| nMOS | 1.32 | 580 | 451 | 0 | 0 | direct with $\lambda_c = 0$ |
| nMOS | 1.32 | 591 | 447 | 0 | 0 | curve fitting with $\lambda_c = 0$ |

## 3.5 Comparison with parameters extracted from the EKV 2.6 compact model

We can compare the data with parameters extracted directly from the EKV 2.6 compact model parameter deck. We first load the EKV 2.6 CM parameters.

The fit is less accurate than those obtained above.

We can check including the value of $\lambda_c$. The result is shown in Figure 3.25.

There is almost no change which is understandable for such a long transistor.

© C. Enz under CC BY-NC-SA 

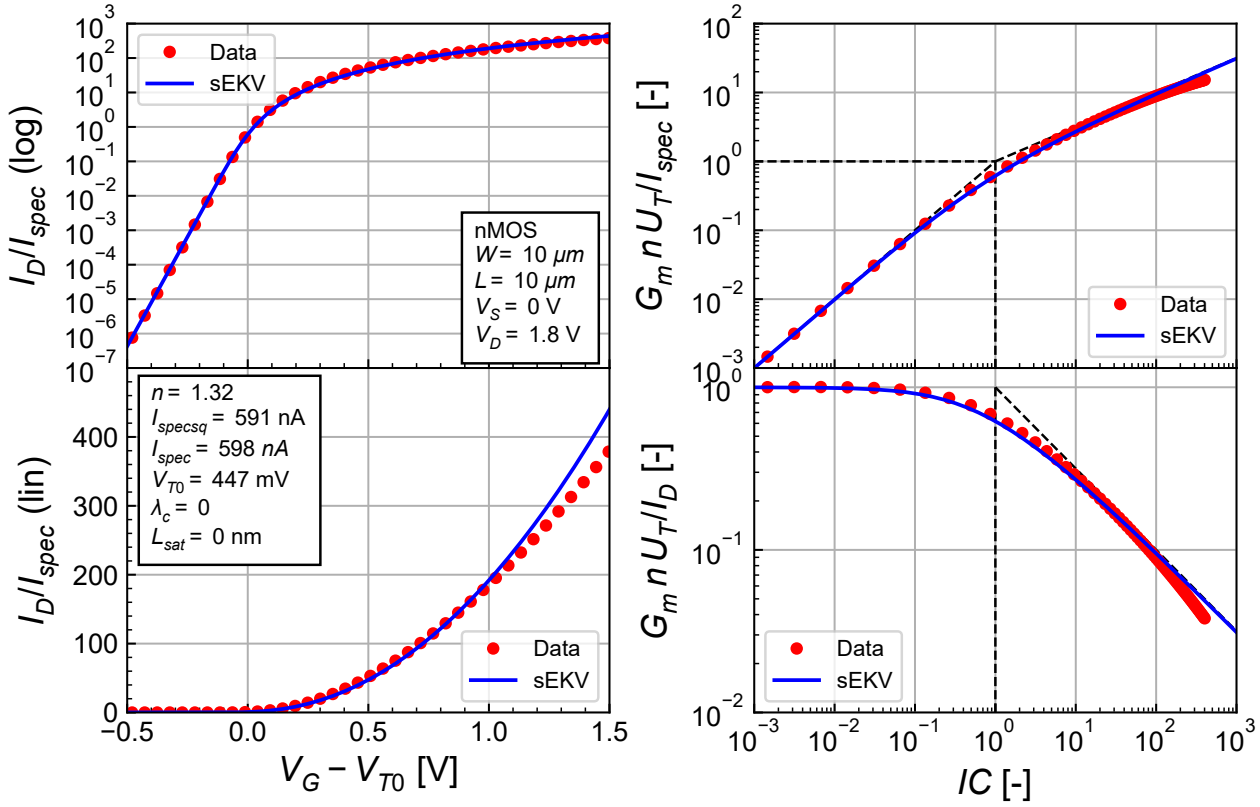



Figure 3.23: Summary of extraction by curve fitting.

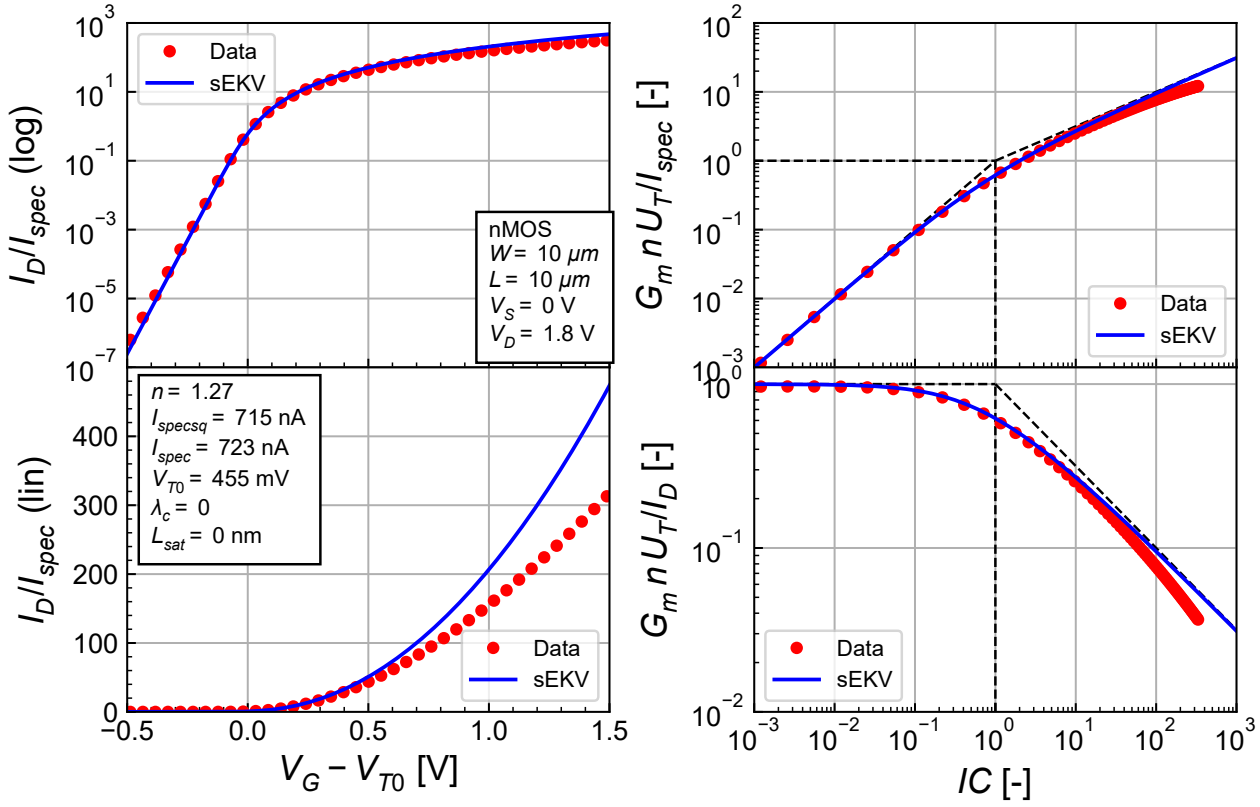



Figure 3.24: Result for the parameters calculated from the EKV 2.6 CM parameters with $\lambda_c = 0$.

© C. Enz under CC BY-NC-SA 

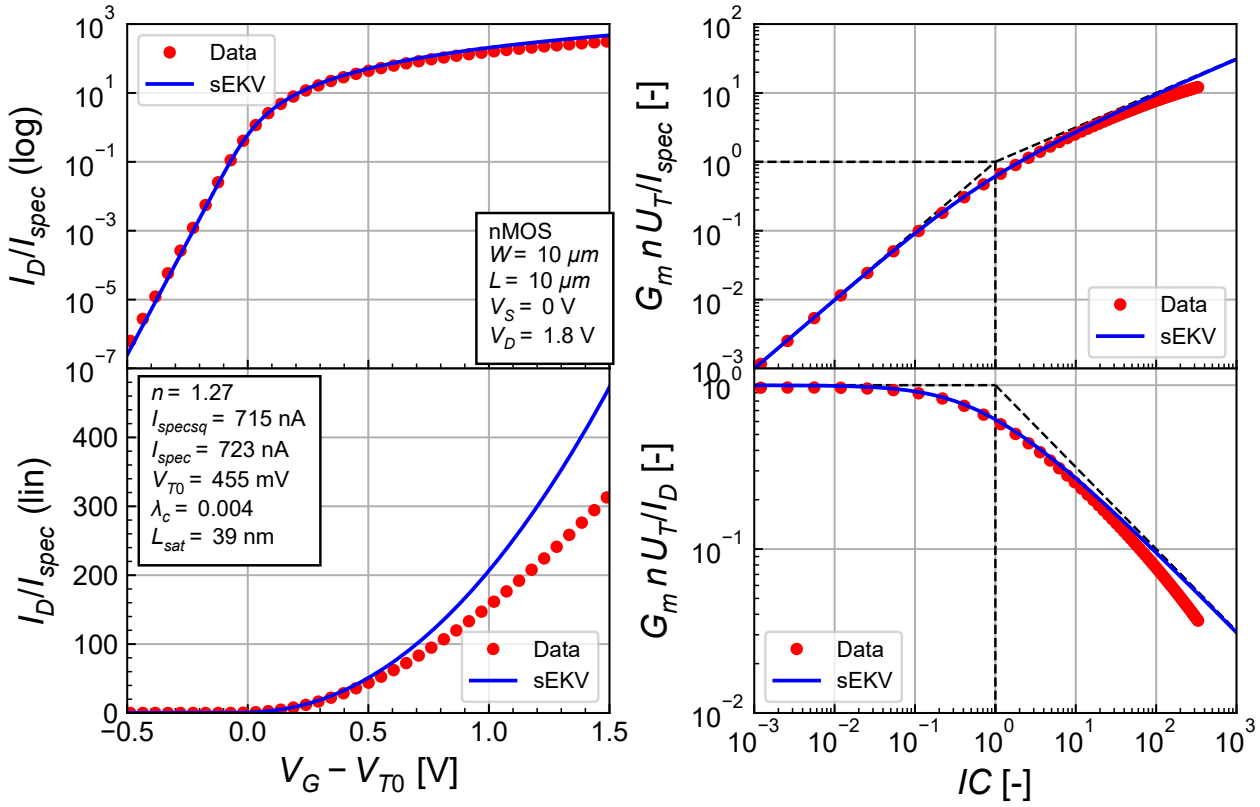



Figure 3.25: Result for the parameters calculated from the EKV 2.6 CM parameters including $\lambda_c$.

Table 3.3: Extraction of the sEKV parameters using curve fitting with $\lambda_c = 0$.

| Type | $n$ | $I_{spec\square}$ $[nA]$ | $V_{T0}$ $[mV]$ | $\lambda_c$ | $L_{sat}$ $[nm]$ | Comment |
|---|---|---|---|---|---|---|
| nMOS | 1.32 | 580 | 451 | 0 | 0 | direct with $\lambda_c = 0$ |
| nMOS | 1.32 | 591 | 447 | 0 | 0 | curve fitting with $\lambda_c = 0$ |
| nMOS | 1.27 | 715 | 455 | 0 | 39 | From EKV 2.6 parameters |

© C. Enz under CC BY-NC-SA 

# 4 Output characteristic

## 4.1 Generating and importing the data

In order to extract the CLM parameter in saturation, we will now filter out the points that correspond to the linear region. We can do this easily by looking at the $G_{ds}$ versus $V_D$ characteristic as shown in Figure 4.3. This done below where we will drop the blue points and keep the red points for the extraction.

### 4.1.1 $I_D$ and $G_{ds}$ versus $V_D$

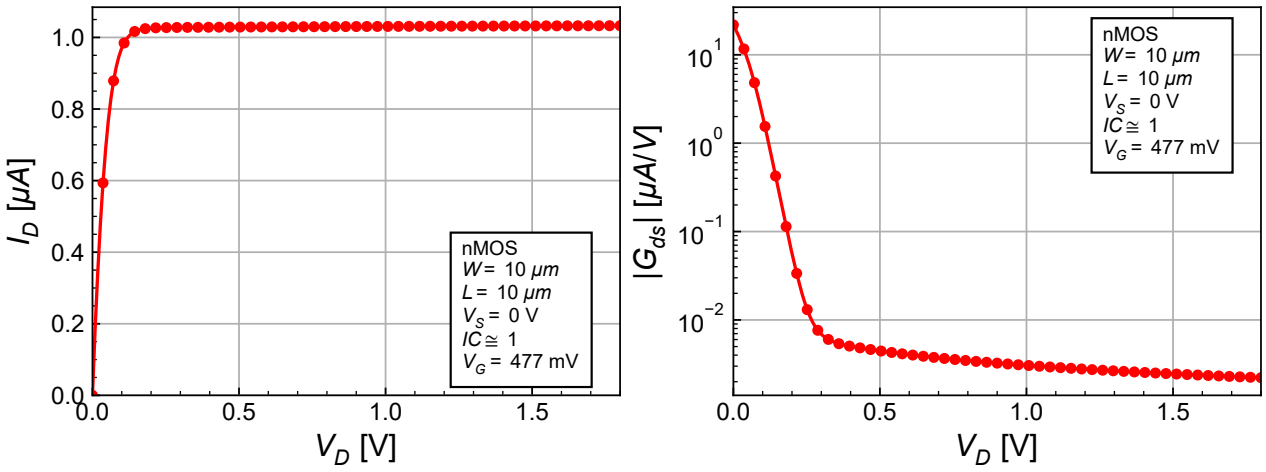



Figure 4.1: Imported $I_D$-$V_D$ and $G_{ds}$-$V_D$.

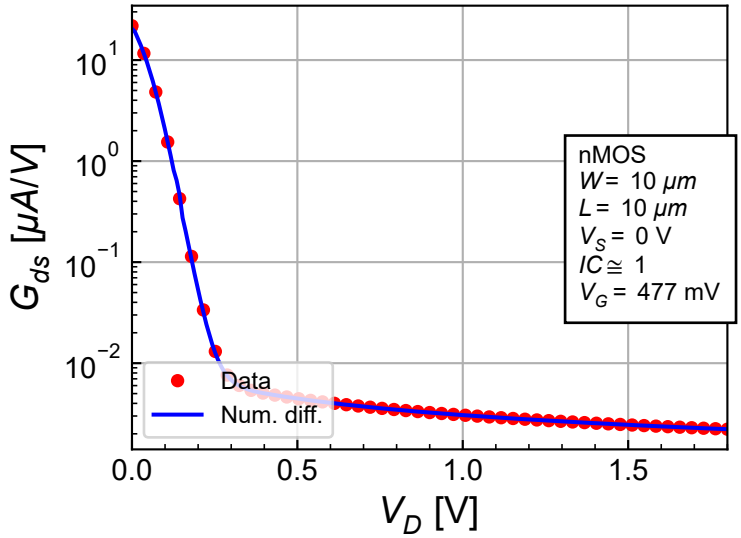



Figure 4.2: Check imported $G_{ds}$ against computed $G_{ds}$.

© C. Enz under CC BY-NC-SA 

The output conductance calculated by differentiating the large-signal $I_D$-$V_D$ matches the value extracted from the PSP model. We will keep the value from PSP.

### 4.1.2 Filtering the outliers

In order to extract the CLM parameter in saturation, we will now filter out the points that correspond to the linear region. We can do this easily by looking at the $G_{ds}$ versus $V_D$ characteristic as shown in Figure 4.3.

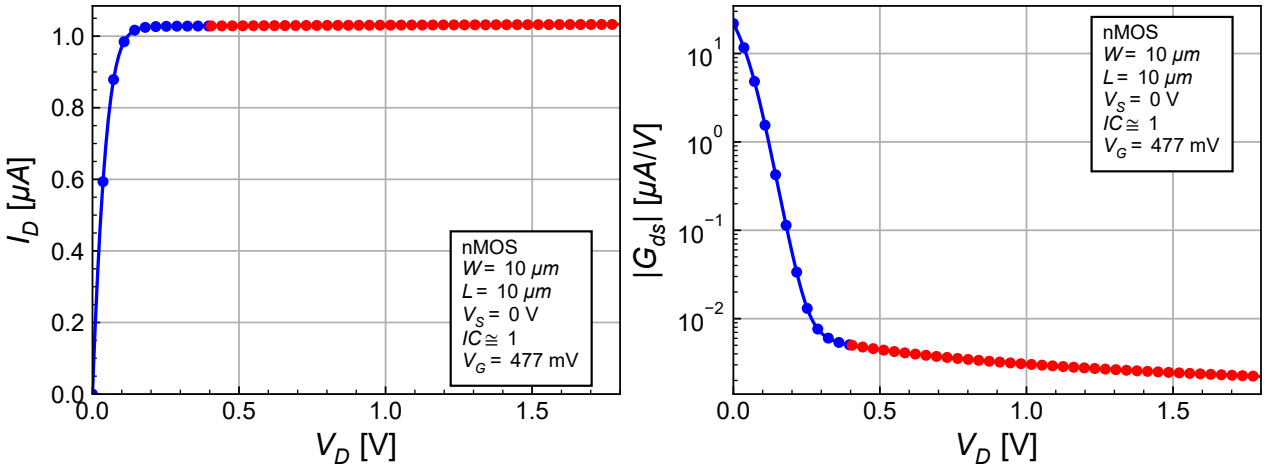



Figure 4.3: Filtering the outliers from $I_D$-$V_G$ and $G_{ds}$-$V_D$.

## 4.2 Extracting the CLM parameter

The simple channel length modulation (CLM) of the output conductance in saturation is approximated by

$$G_{ds} = \frac{I_{D,sat}}{V_E} \tag{4.1}$$

where $I_{D,sat}$ is the drain current in saturation and

$$V_E = \lambda \cdot L_{eff} \tag{4.2}$$

is the Early voltage or CLM voltage which is proportionnal to the effectve length. This corresponds to a linear approximation of the drain current in saturation given by

$$I_{D,sat} \cong G_{ds} \cdot (V_D - V_E) \tag{4.3}$$

The value $I_{D0}$ corresponds to the intercept

$$I_{D0} = -G_{ds} \cdot V_E \tag{4.4}$$

which is positive since $V_E$ is negative.

As shown in the right plot of Figure 4.4, the output conductance is approximated by a constant value represented by the dashed black line. It is a poor approximation of the output conductance but good enough for starting a design. Note that, in analog circuit design, having a good fit of the output conductance is less important than having a good fit of the transconductance because often we just need the intrinsic voltage gain to be large enough for the circuit to perform correctly, while we want to have a good estimation of the parameters depending on the transconductance, such as the gain-bandwidth product or the thermal noise.

© C. Enz under CC BY-NC-SA 

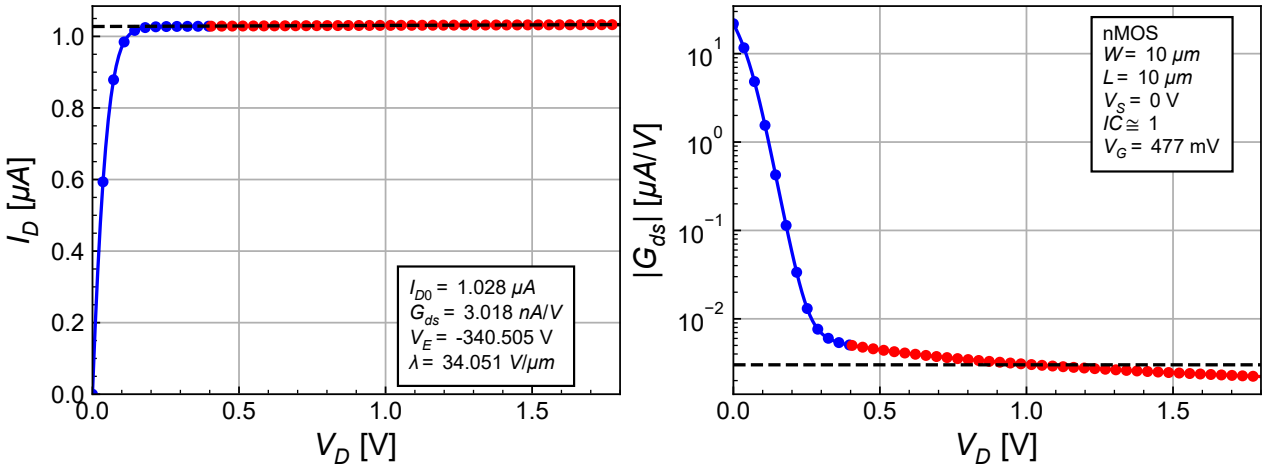



Figure 4.4: Extraction of the CLM parameter $\lambda$.

Table 4.1: CLM parameters extracted in moderate inversion.

| Type | $L_{eff}$ [$\mu m$] | $IC$ | $G_{ds}$ [$nA/V$] | $I_{D0}$ [$\mu A$] | $V_E$ [$V$] | $\lambda$ [$V/\mu m$] | Comment |
|---|---|---|---|---|---|---|---|
| nMOS | 9.924 | 1 | 3.018 | 1.028 | -340.505 | 34.051 | moderate |

© C. Enz under CC BY-NC-SA 

# 5 Noise

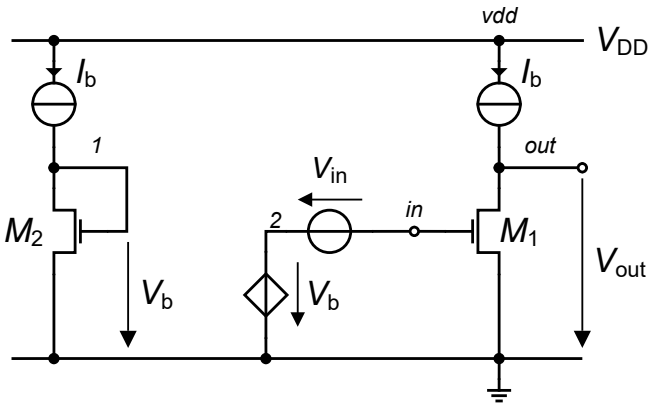



Figure 5.1: Schematic used for the noise simulation.

We now will check the noise model including the thermal and flicker noise. The simulations will be performed with the help of the schematic shown in Figure 5.1. Transistor $M_1$ is the active transistor and $M_2$, which is identical to $M_1$, is used to set the gate voltage of $M_1$ such that its current is equal to $I_b$.

## 5.1 Setting the bias conditions

Table 5.1: Transistor size and bias information.

| Transistor | $W\ [\mu m]$ | $L\ [\mu m]$ | $I_D\ [nA]$ | $I_{spec}\ [nA]$ | $IC$ | $V_G - V_{T0}\ [mV]$ | $V_{DSsat}\ [mV]$ |
|---|---|---|---|---|---|---|---|
| M1 | 10.00 | 10.00 | 723 | 724 | 1.0 | 15 | 116 |
| M2 | 10.00 | 10.00 | 723 | 724 | 1.0 | 15 | 116 |

We choose an inversion coefficient $IC = 1$, which for the selected transistor size leads to a bias current $I_b = 0.723\ \mu A$.

Table 5.2: Transistor small-signal and thermal noise parameters.

| Transistor | $G_{spec}\ [\mu A/V]$ | $G_{ms}\ [\mu A/V]$ | $G_m\ [\mu A/V]$ | $G_{ds}\ [nA/V]$ | $\gamma_n$ |
|---|---|---|---|---|---|
| M1 | 27.984 | 17.281 | 13.593 | 2.140 | 0.717 |
| M2 | 27.984 | 17.281 | 13.593 | 2.140 | 0.717 |

## 5.2 Extract operating point information

The node voltages are given in Table 5.3.

© C. Enz under CC BY-NC-SA 

Table 5.3: Node voltages.

| Node | Voltage |
|---|---|
| vdd | 1.8 |
| in | 0.479711 |
| out | 0.479711 |
| 1 | 0.479711 |
| 2 | 0.479711 |
| 1 | 0.479711 |

Table 5.4: Operating point information extracted from ngspice .op file for each transistor.

| Transistor | $I_D$ $[nA]$ | $I_{spec}$ $[nA]$ | $IC$ | $n$ | $V_{Dsat}$ $[mV]$ |
|---|---|---|---|---|---|
| M1 | 723 | 706 | 1.025 | 1.27 | 156 |
| M2 | 723 | 706 | 1.025 | 1.27 | 156 |

Table 5.5: Small-signal operating point information extracted from ngspice .op file for each transistor.

| Transistor | $G_m$ $[\mu A/V]$ | $G_{ms}$ $[\mu A/V]$ | $G_{ds}$ $[nA/V]$ |
|---|---|---|---|
| M1 | 13.258 | 17.079 | 3.319 |
| M2 | 13.258 | 17.079 | 3.319 |

Table 5.6: Noise operating point information extracted from ngspice .op file for each transistor.

| Transistor | $R_n$ $[k\Omega]$ | $\sqrt{S_{ID,th}}$ $[nA/\sqrt{Hz}]$ | $\gamma_n$ [-] | $\sqrt{S_{ID,fl}}$ at 1Hz $[nA/\sqrt{Hz}]$ |
|---|---|---|---|---|
| M1 | 55.659 | 30.375 | 0.738 | 3100.05 |
| M2 | 55.659 | 30.375 | 0.738 | 3100.05 |

## 5.3 Input-referred noise PSD

To compare the simulated noise to the theoretical noise PSD, we can simulate the circuit shown in . The noise at the output- and input-referred noise PSD will include both contributions of $M_1$ and $M_2$. SInce $M_1$ are identical and have the same bias current, we can simply divide the output- and inputreferred noise PSD by a factor 2. In ngspice to get the noise PSD we need to set `setplot noise1`. We can then export the noise data using `wrdata $inputdir/noise.nz.dat inoise_spectrum onoise_spectrum`. The simulated input-referred noise PSD is compared to the theoretical one in Figure 5.2.

We can extract the individual contributions of $M_1$ by the following instrauctions `save onoise_n1 onoise_n1_flicker onoise_n1_thermal` and saving the raw data with `write $inputdir/noise.nz.raw`. The resulting PSD are plotted in Figure 5.3.

We see that the simulation matches the theoretical estimation, particularly for the flicker noise. The simulated thermal noise is slightly larger than the theoretical estimation. This comes from the slightly smaller simulated transconductance compared to the theoretical value.

© C. Enz under CC BY-NC-SA 

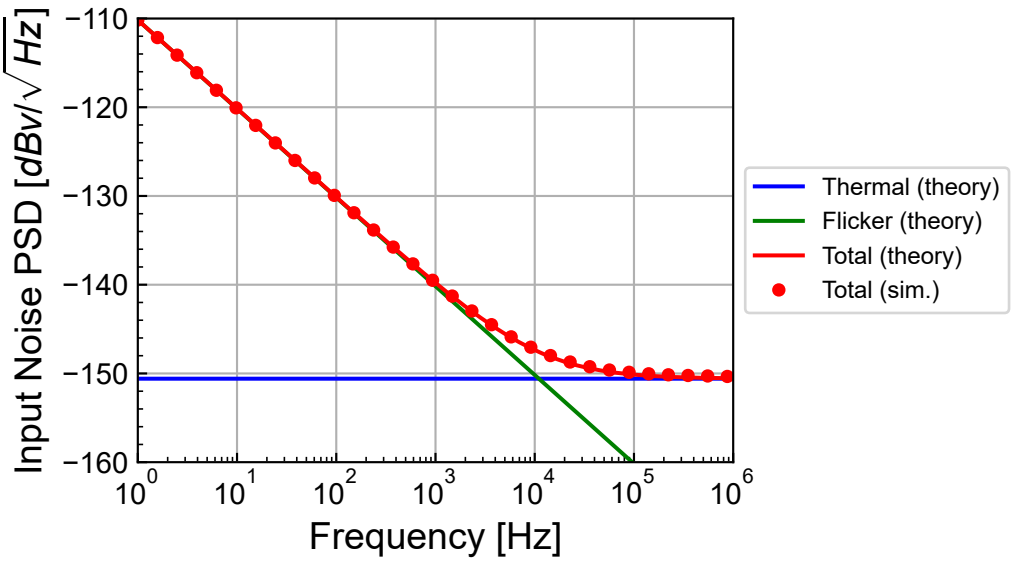



Figure 5.2: Simulated input-referred noise PSD of $M_1$ compared to theoretical estimation from `inoise_spectrum`.

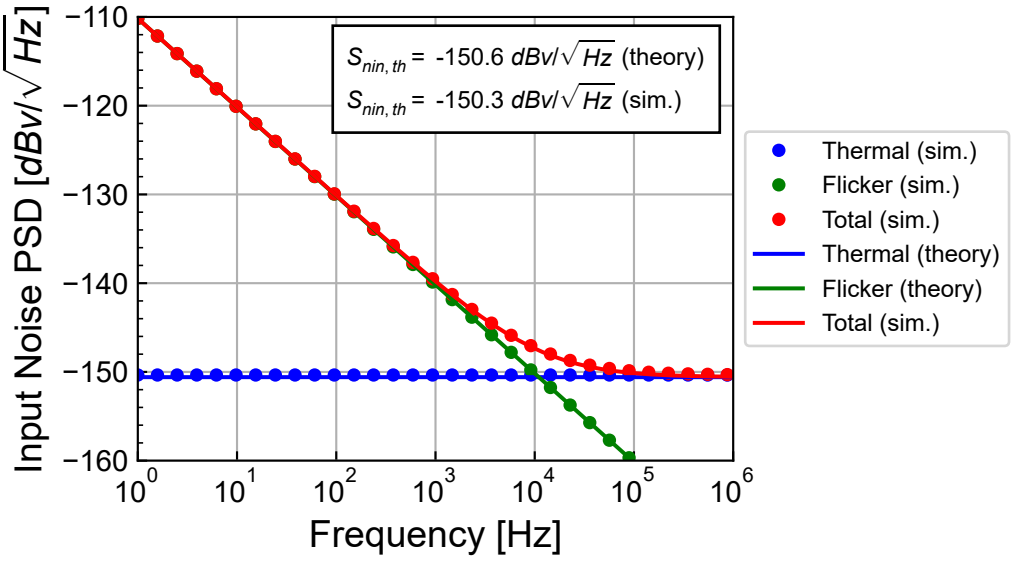



Figure 5.3: Simulated input-referred noise PSD of $M_1$ compared to theoretical estimation.

© C. Enz under CC BY-NC-SA 

# 6 Conclusion

This notebook presented different approaches to extract the sEKV parameters for a long-channel nMOS transistor for a generic 180nm bulk CMOS technology. The data was first obtained by simulations using the EKV 2.6 compact model.

The sEKV parameters were first extracted using a direct extraction methodology with $\lambda_c = 0$. This results in a good fit over all regions of operation except in very strong inversion because effect of mobility reduction due to the vertical field is not included in the sEKV model. Things can be improved by using the $\lambda_c$ parameter to account for this effect although this is a very long-channel transistor.

Overall we have shown that sEKV can fit the large- and small-signal data of this is a long-channel nMOS transistor very well.

*© C. Enz under CC BY-NC-SA* 

# References

[1] C. C. Enz and E. A. Vittoz, *Charge-Based MOS Transistor Modeling - The EKV Model for Low-Power and RF IC Design*, 1st ed. John Wiley, 2006.

[2] C. Enz, F. Chicco, and A. Pezzotta, "Nanoscale MOSFET Modeling: Part 1: The Simplified EKV Model for the Design of Low-Power Analog Circuits," *IEEE Solid-State Circuits Magazine*, vol. 9, no. 3, pp. 26–35, 2017.

[3] Han, H.-C. and A. D'Amico and C. Enz, "SEKV-E: Parameter Extractor of Simplified EKV I-V model for Low-power Analog Circuits." https://gitlab.com/moscm/sekv-e, 2022.

[4] H.-C. Han, A. D'Amico, and C. Enz, "SEKV-E: Parameter Extractor of Simplified EKV I-V Model for Low-Power Analog Circuits," *IEEE Open Journal of Circuits and Systems*, vol. 3, pp. 162–167, 2022.

[5] M. Bucher, C. Lallement, C. Enz, F. Theodoloz, and F. Krummenacher, "The EPFL-EKV MOSFET Model Equations for Simulation." https://github.com/chrisenz/EKV/blob/main/EKV2.6/docs/ekv_v26_rev2.pdf, 1998.

*© C. Enz under CC BY-NC-SA* 